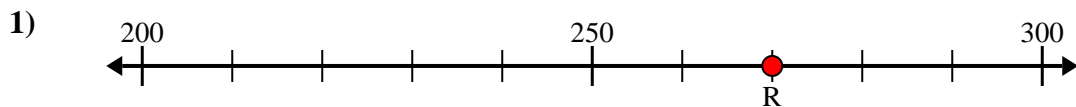





Find the value of R.


Answers




1. \_\_\_\_\_

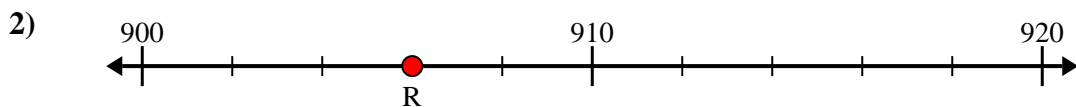


2. \_\_\_\_\_

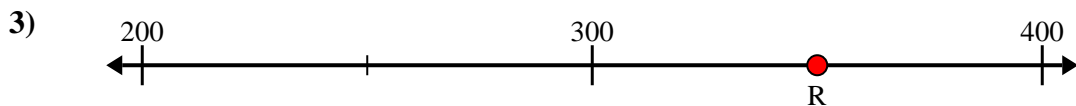


3. \_\_\_\_\_

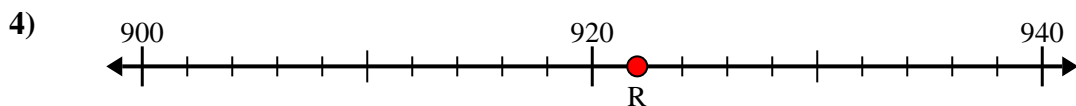


4. \_\_\_\_\_

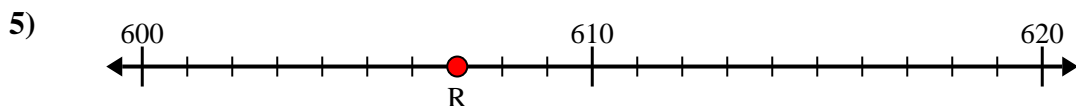


5. \_\_\_\_\_

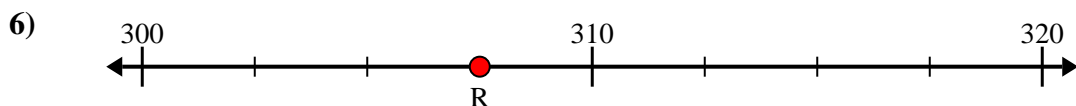


6. \_\_\_\_\_

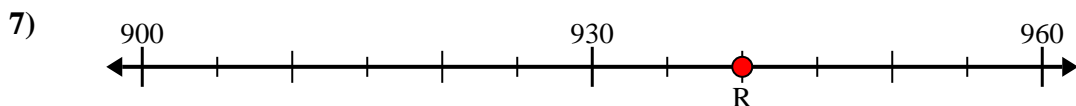


7. \_\_\_\_\_

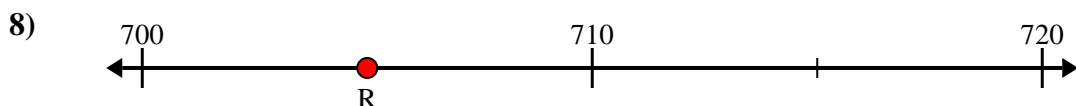

8. \_\_\_\_\_

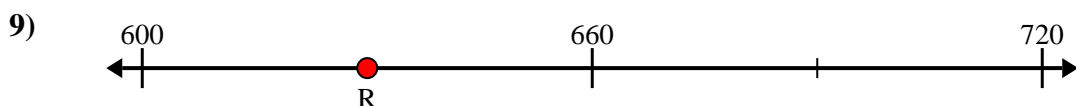











9. \_\_\_\_\_

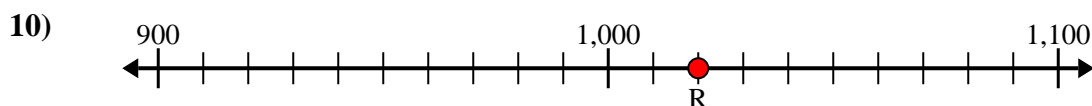

10. \_\_\_\_\_



Find the value of R.

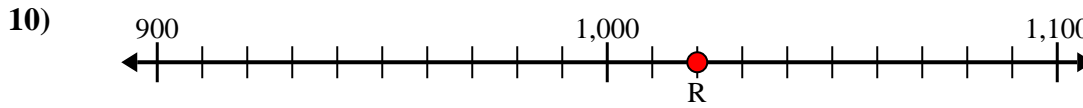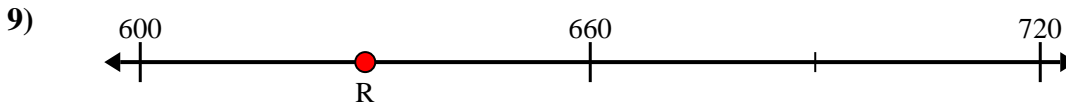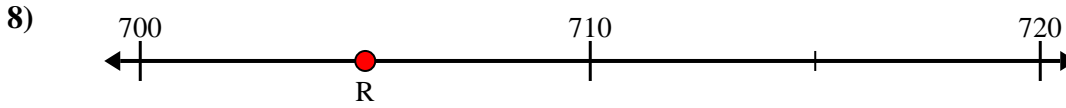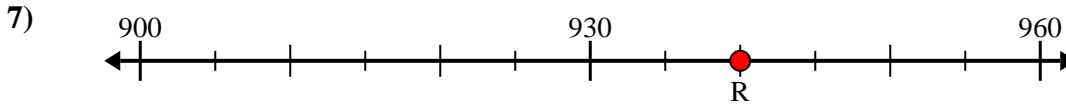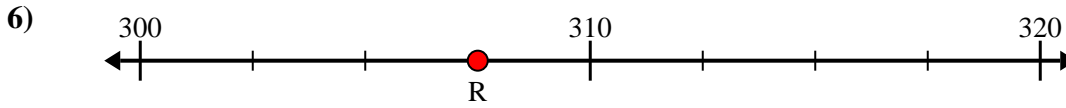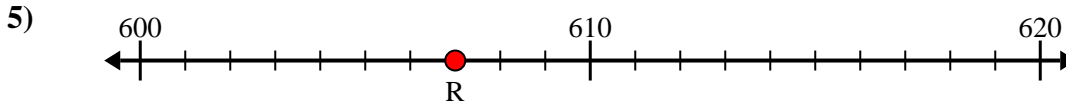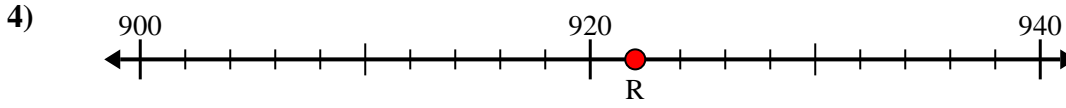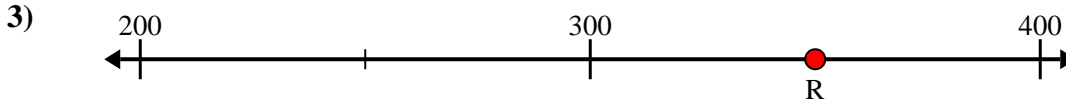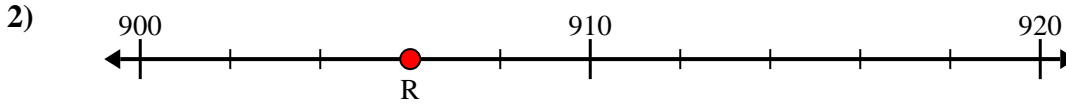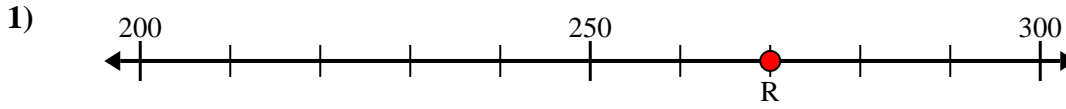

Answers

1. 270

2. 906

3. 350

4. 922

5. 607

6. 307.5

7. 940

8. 705

9. 630

10. 1,020